

CADD JOB ASSIGNMENT

NAME: ARAVIND AKSHIT NITTALA

SRN: PES2UG23EC026

SECTION: 3RD SEM A SECTION

1. Floating Point Multiplier

(a) Steps for 32-bit Floating Point Multiplication

Extract Fields: Extract the sign, exponent, and mantissa from both 32-bit floating-point inputs.

Sign Calculation: XOR the sign bits of the two inputs to get the sign of the result.

Exponent Calculation: Add the exponents of the two inputs and subtract the bias (127 for single precision).

Mantissa Calculation: Multiply the mantissas of the two inputs. Normalize the result if necessary.

Normalization: Adjust the exponent and mantissa to ensure the mantissa is in the correct range.

Rounding: Apply round toward zero (truncate).

Assemble Result: Combine the sign, exponent, and mantissa to form the final 32-bit floating-point result.

System Verilog design code for floating point multiplier

```
module fp_multiplier (  
    input [31:0] a,  
        input [31:0] b,  
    output [31:0] result  
);  
    wire sign_a, sign_b, sign_result;  
    wire [7:0] exp_a, exp_b, exp_result;  
    wire [23:0] mant_a, mant_b, mant_result;  
    wire [47:0] mant_mult;  
    wire [7:0] exp_sum;  
  
    assign sign_a = a[31];  
    assign sign_b = b[31];  
    assign exp_a = a[30:23];  
    assign exp_b = b[30:23];  
    assign mant_a = {1'b1, a[22:0]};  
    assign mant_b = {1'b1, b[22:0]};  
  
    assign sign_result = sign_a ^ sign_b;  
    assign exp_sum = exp_a + exp_b - 8'd127;  
    assign mant_mult = mant_a * mant_b;  
  
    assign mant_result = mant_mult[47] ? mant_mult[46:24] : mant_mult[45:23];  
    assign exp_result = mant_mult[47] ? exp_sum + 1 : exp_sum;  
  
    assign result = {sign_result, exp_result, mant_result[22:0]};  
endmodule  
  
input [31:0] a,  
    input [31:0] b,  
output [31:0] result  
);  
    wire sign_a, sign_b, sign_result;  
    wire [7:0] exp_a, exp_b, exp_result;  
    wire [23:0] mant_a, mant_b, mant_result;  
    wire [47:0] mant_mult;  
    wire [7:0] exp_sum;
```

```
assign sign_a = a[31];
assign sign_b = b[31];
assign exp_a = a[30:23];
assign exp_b = b[30:23];
assign mant_a = {1'b1, a[22:0]};
assign mant_b = {1'b1, b[22:0]};

assign sign_result = sign_a ^ sign_b;
assign exp_sum = exp_a + exp_b - 8'd127;
assign mant_mult = mant_a * mant_b;

assign mant_result = mant_mult[47] ? mant_mult[46:24] : mant_mult[45:23];
assign exp_result = mant_mult[47] ? exp_sum + 1 : exp_sum;

assign result = {sign_result, exp_result, mant_result[22:0]};
endmodule
```

Testbench

```
module test_fp_multiplier;
  logic [31:0] a, b;
  logic [31:0] result;

  fp_multiplier uut (
    .a(a),
    .b(b),
    .result(result)
  );

  initial begin
    $display("Time\t a\t\t b\t\t result");
    $monitor("%0t\t %h\t %h\t %h", $time, a, b, result);

    // Test cases
    a = 32'h3f800000; // 1.0
    b = 32'h40000000; // 2.0
    #10;




    a = 32'h40400000; // 3.0
    b = 32'h40800000; // 4.0
    #10;

    a = 32'h3f800000; // 1.0
    b = 32'h3f800000; // 1.0
    #10;

    a = 32'h3f800000; // 1.0
    b = 32'h00000000; // 0.0
    #10;

    a = 32'h3f800000; // 1.0
    b = 32'hbf800000; // -1.0
    #10;

    $finish;
  end
endmodule
```

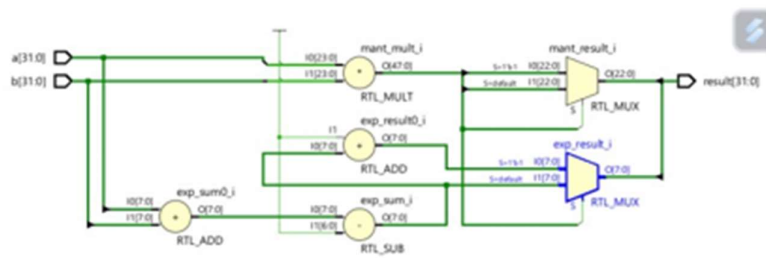 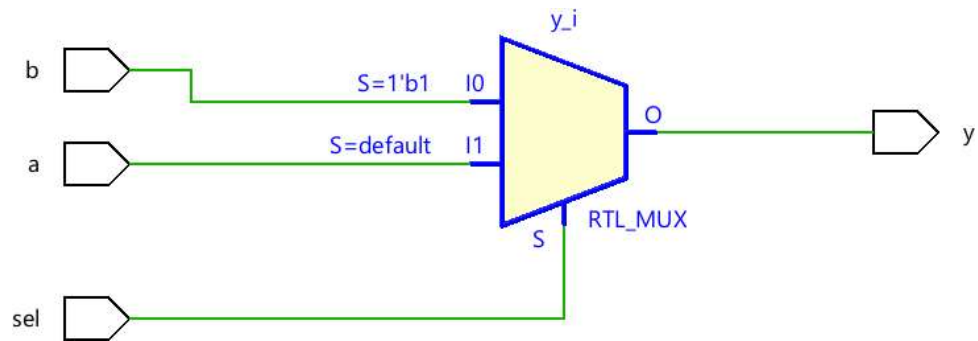

32-bit prefix adder

Input A -> Input B -> Generate & Propagate -> Prefix Tree -> Sum Calculation -> Output Sum.

System Verilog design code for 32-prefix adder

```
module prefix_adder (  
    input [31:0] a,  
    input [31:0] b,  
    output [31:0] sum  
);  
    wire [31:0] g, p, c;  
  
    assign g = a & b;  
    assign p = a ^ b;  
  
    assign c[0] = 0;  
    genvar i;  
    generate  
        for (i = 1; i < 32; i = i + 1) begin  
            assign c[i] = g[i-1] | (p[i-1] & c[i-1]);  
        end  
    endgenerate  
  
    assign sum = p ^ c;  
endmodule
```

testbench

```
module test_prefix_adder;  
    logic [31:0] a, b;  
    logic [31:0] sum;  
  
    prefix_adder uut (  
        .a(a),  
        .b(b),
```

```

        .sum(sum)
    );

    initial begin
        $display("Time\t a\t\t b\t\t sum");
        $monitor("%0t\t %h\t %h\t %h", $time, a, b, sum);

        // Test cases
        a = 32'h00000000; b = 32'h00000000; #10;
        a = 32'h00000001; b = 32'h00000001; #10;
        a = 32'hFFFFFFF; b = 32'h00000001; #10;
        a = 32'h12345678; b = 32'h87654321; #10;
        a = 32'hAAAAAAAA; b = 32'h55555555; #10;

        $finish;
    end
endmodule

```

Delay Calculation

The delay of the 32-bit prefix adder can be calculated based on the number of stages in the prefix tree. Assuming each two-input gate delay is 100 ps, the delay can be estimated by counting the number of stages

pipelined prefix adder

```

module pipelined_prefix_adder (
    input clk,
    input [31:0] a,
    input [31:0] b,
    output reg [31:0] sum
);
    reg [31:0] g, p, c;

    always @(posedge clk) begin
        g <= a & b;
        p <= a ^ b;
    end
endmodule

```


end

```
always @(posedge clk) begin
    c[0] <= 0;
    for (int i = 1; i < 32; i = i + 1) begin
        c[i] <= g[i-1] | (p[i-1] & c[i-1]);
    end
end
```

```
always @(posedge clk) begin
    sum <= p ^ c;
end
endmodule
```

